

CS-223
Digital Design
Section: 3
PROJECT REPORT
Programmable Processor


Mehmet Hasat Serinkan 21901649 09.05.2022

 
B) RTL schematics for Multiplication and Division operations



 

D) Controller Block Diagram

 

 

F) Testbenches

```
`timescale lns / lps
module testbench2();
logic clk, load;
logic [11:0] in, out;
instructionRegister dut(clk, load, in, out);
always
   begin
       clk <= 1; # 5; clk <= 0; # 5;
initial begin
       load = 0;
        in = 12'b101010000001; # 10;
        in = 12'b110010000001; # 10;
        load = 1;
        in = 12'b100100100000; # 10;
        in = 12'b010010101001; # 10;
        in = 12'b000000010010; # 10;
        in = 12'b000110010010; # 10;
        in = 12'b001000010100; # 10;
        in = 12'b101010000001; # 10;
        in = 12'b110010000001; # 10;
        in = 12'b010000000000; # 10;
        in = 12'b011000000000; # 10;
        in = 12'b100000000000; # 10;
        in = 12'b100000000011; # 10;
        in = 12'b010010101000; # 10;
       in = 12'b010110100000; # 10;
        in = 12'b000000011000; # 10;
    end
endmodule
```

```
1 'timescale lns / lps
2 	☐ module testbenchl();
3 logic clk, write, read,clr;
4 logic [3:0] address;
5 logic [3:0] data;
6 logic [3:0] out;
7 dataMemory dut (clk, clr, read, write, address, data, out );
8 always
9 🖯
       begin
10
        clk <= 1; # 5; clk <= 0; # 5;
      end
12
13 🖯 initial begin
14 | write = 1; read = 0; clr = 1;
15
     data = 4'b0000; address = 4'b0000;
16 :
    #10;
17 clr = 0;
18
    data = 4'b0010; address = 4'b0001;
19
    #10;
20
    data = 4'b0100; address = 4'b0010;
21
     #10;
22
    data = 4'b0110; address = 4'b0011;
    #10;
23 :
24
     data = 4'b1000; address = 4'b0100;
25 #10;
26
    data = 4'b1010; address = 4'b0101;
27
     #10;
28
    data = 4'b1100; address = 4'b0110;
29
    #10;
     data = 4'b1110; address = 4'b0111;
30
31
    #10;
32
    data = 0; read = 1; write = 0;
    data = 4'b0000; address = 4'b0000;
33
34
35 data = 4'b0010; address = 4'b0001;
35 | data = 4'b0010; address = 4'b0001;
36 #10;
37
      data = 4'b0100; address = 4'b0010;
38
      #10;
39
      data = 4'b0110; address = 4'b0011;
40
41
      data = 4'b1000; address = 4'b0100;
42
      #10;
43 data = 4'b1010; address = 4'b0101;
44 #10;
45 data = 4'b1100; address = 4'b0110;
46
     #10;
47
     data = 4'b1110; address = 4'b0111;
48
     #10;
49 A end
50
51 @ endmodule
```